
NAME: MAHAD SHAHNAWAZ


ROLL NO. : 24K-3057


DLD LAB TASK 6:

QUESTION: 02

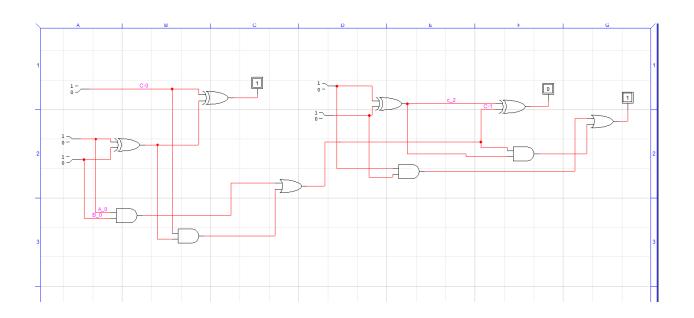

QUESTION: 03

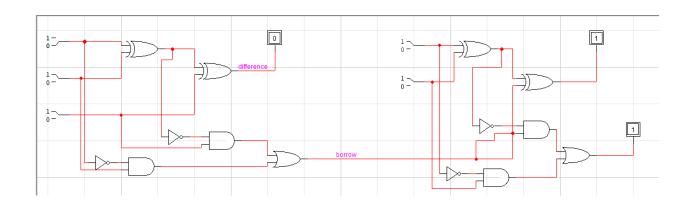

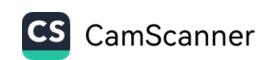

| | Date | d: | | LAB | WORK | |
|---|------|---------------------------|-----------------------|-----|-------|--|
| a | 10: | 1 | | | | 6 |
| | | | | | | 6 |
| | A | В | C | Sum | Carry | |
| | 0 | 0 | 0 | 0 | 0 | - |
| | 0 | 0 | 1 | 1 | 0 | • |
| | 0 | 1 | 0 | 1 | 0 | 9 |
| | 0 | 1 | 1 | 0 | 1 | |
| | 1 | 0 | 0 | 1 | 0 | |
| | 1 | 0 | 1 | 0 | 1 | |
| | 1 | 1 | 0 | 0 | 1 | |
| | 1 | 1 | 1 | 1 | | The state of the s |
| | (| 18 C (10) (1) (1) (1) (1) | 0 | | * -) | 00 01 01 11 00 11 10 10 10 10 10 10 10 1 |
| | 001 | | ABC | | | i) $011 + 111 = $ $ABC + ABC = $ BC ii) $110 + 111 = $ $ABC + ABC = $ AB $111 + 101 = $ $ABC + ABC = $ AC |
| | | | + \$\$\$ + - ABC + | | | AB + BC + AC |

